

Assignment # 3

(CLO3-P1)

Q1: **Select** appropriate port interfacing instructions to control the load in the following circuit. The load should be ON at reset. Additionally, add a switch at RA1 to turn on/off the load when desired?

